

Lab 6 Report: Live-Time Audio Visualizer

Hunter North and Peter Zhong

EE 371

Jun 2, 2021

Procedure

Lab 6 asked us to implement a project of our own with at least one input device and at least one output device. After some discussion between the group members, we decided to implement a live-time audio visualiser on FPGA. This visualizer takes an mp3 audio file as input, and outputs the average amplitude of the audio as colored bars with different heights moving across the VGA display.

Here are some module-by-module specifications of our live-time audio visualizer project:

- The width of the bars are fixed to 29 pixels with 2-pixel gaps (see “DE1_SoC.sv”).

 


Figure 1. DE1_SoC Block Diagram. Image showing the correct input and output signals required to drive the top-level module.

- The heights of the bars are the average amplitude of the audio scaled down linearly to fit the 480 vertical pixels on the VGA display (see “height_picker.sv”).

 


Figure 2. height_picker Block Diagram. Image showing the correct input and output signals required to drive the height_picker module.

- The RGB values of the colors of the bars are respectively determined by the first 8 bits, second 8 bits, and third 8 bits of the average amplitude of the audio (see “color_picker.sv”).

 


Figure 3. color_picker Block Diagram. Image showing the correct input and output signals required to drive the color_picker module.

- The RGB values and the heights of the bars are synchronously updated to the top-level module with a bar drawer module (see “bar_drawer.sv”).

 


Figure 4 bar_drawer Block Diagram. Image showing the correct input and output signals required to drive the bar_drawer module.

- The updating frequency of the average amplitude of the bar and the number of samples to take the average amplitude of is determined by the parameter UPDATE_FREQ in the audio averaging module. The average values of the samples are shifted across the bars through a shift register implemented with an always_ff block (see “audio_averaging_shifting.sv”).

 


Figure 5. audio_averaging_shift Block Diagram. Image showing the correct input and output signals required to drive the audio_averaging_shift module.

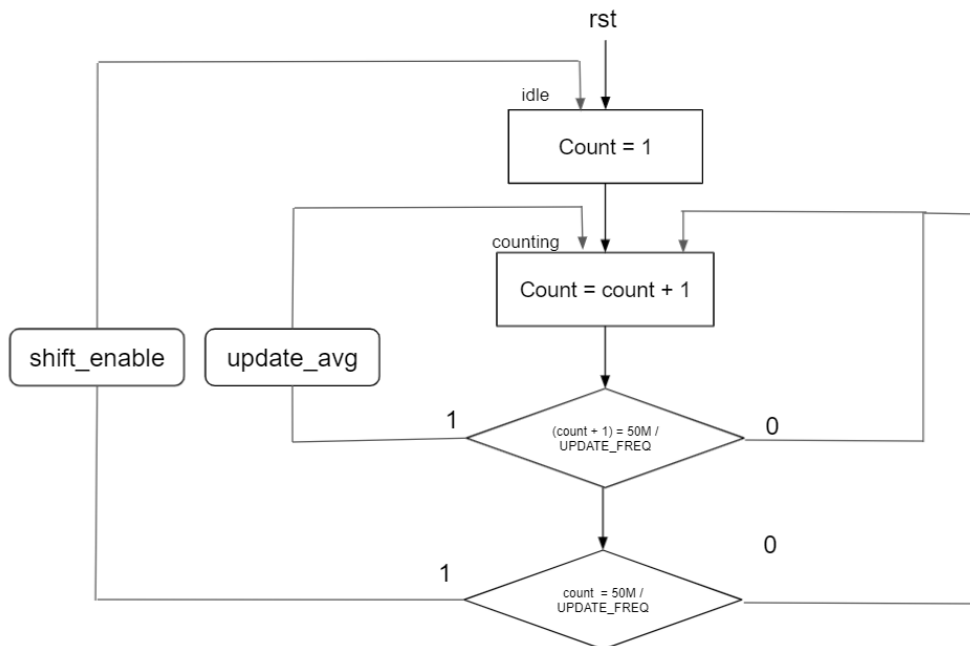


Figure 6. ASMD chart for the control signals in the audio_averaging_shift module

Lastly, we went about wiring up all of these modules together. We created the audio averaging shift module and wired each output to its own bar_drawer module. Each bar_drawer module holds a color and height picker which decide the characteristics of the audio bar. The desired information is utilized by the video driver to paint an image on the VGA monitor.

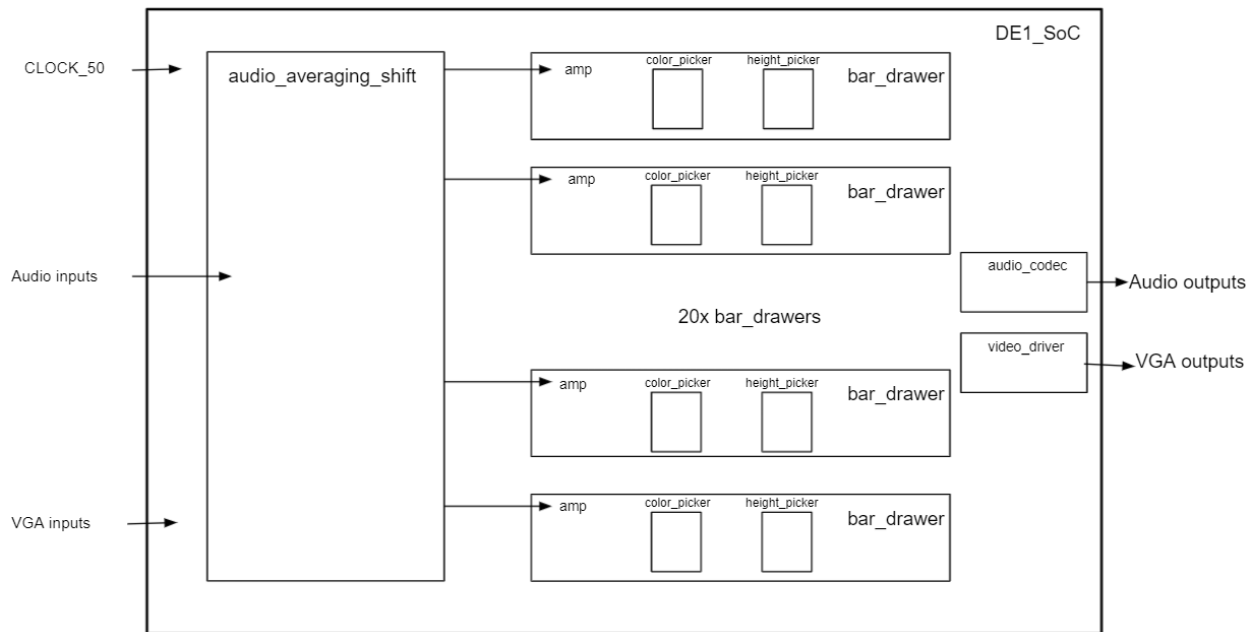


Figure 7. System Structure. Diagram that shows how all the individual modules are wired together in order to build the Live Time Audio Visualizer.

Results

height_picker.sv

This waveform below (Figure 8) shows the successful testing of the height_picker module. In order to test the functionality of the height_picker module, we picked three random 24-bit numbers and passed them into the module. As can be seen from the waveform below, the height_picker module successfully scaled the 24-bit numbers down to a number between 0 and 480.

 


Figure 8. height_picker testbench. Testbench that is run to confirm that the height_picker module is functioning correctly.

color_picker.sv

This waveform below (Figure 9) shows the successful testing of the color_picker module. In order to test the functionality of the color_picker module, we picked three random 24-bit numbers to be the average amplitude of audio, and passed them into the module. As can be seen from the waveform below, the color_picker module successfully determined the RGB values of the colors of the bars through the first, second and third 8 bits of the 24-bit numbers.

 


Figure 9. color_picker testbench. Testbench that is run to confirm that the color_picker module is functioning correctly.

bar_drawer.sv

This waveform below (Figure 10) shows the successful testing of the bar_drawer module. In order to test the functionality of the bar_drawer module, we tested a medium sized amplitude of 8 million. We began by resetting the module, and passed the amplitude value into the module. We also tested the case when the VGA driver is drawing pixels that are outside of the height of the current bar. As can be seen from the waveform below, the bar_drawer module returns the correct color when the currently drawn pixel is within the height of the bar, and returns all zeros when the pixel is out of range to draw black.

 


Figure 10. bar_drawer testbench. Testbench that is run to confirm that the color_picker module is functioning correctly.

audio_averaging_shift.sv

This waveform below (Figure 11) shows the successful testing of the `audio_averaging_shift` module. In order to test the functionality of the `audio_averaging_shift` module, we set the dut's updating frequency to once every 5 clock cycles, and passed a sequence of random input amplitude values into the module. As can be seen from the waveform below, the module successfully computes the average value of the previous amplitudes and updates the most recent average value before shifting it into the shift registers used to support the `bar_drawers` modules

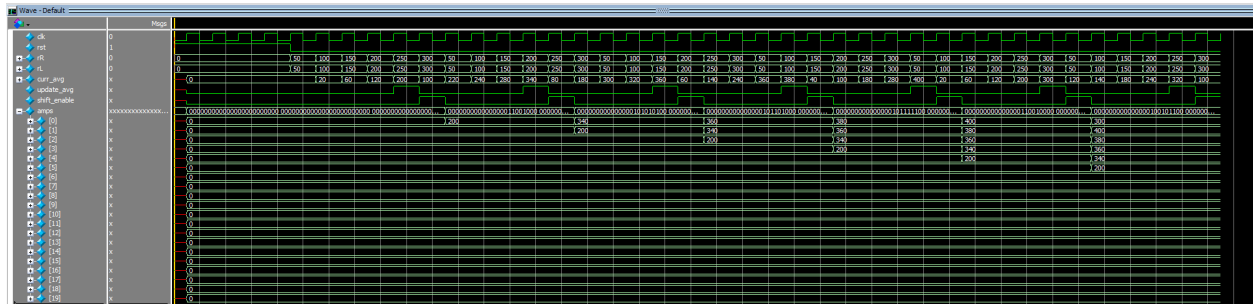


Figure 11. Waveform generated by Appendix 1.E that demonstrates a successful test of the `audio_averaging_shift` module.

Appendix

1.A - DE1_SoC.sv

```
1 // Hunter North and Peter Zhong
2 // 05/26/2021
3 // EE 371
4 // Lab 6
5 //
6 // Top level module which will create the live time audio visualizer
7 // Parameters required:
8 // HEX - 7 bit structures representing hex displays on the DE1_SoC
9 // KEY - 4 different signals representing the press on a key button on a DE1_SoC
10 // LEDR - 10 different signals representing the LEDs on DE1_SoC
11 // SW - 10 different signals representing the switches on the DE1_SoC
12 // CLOCK_50 - 50 Mhz clock signal
13 // VGA drivers - A set of drivers used to make the VGA function
14 // Audio drivers - A set of drivers used to make the audio function
15 //
16 module DE1_SoC (HEX0, HEX1, HEX2, HEX3, HEX4, HEX5, KEY, LEDR, SW,
17                CLOCK_50, CLOCK2_50, VGA_R, VGA_G, VGA_B, VGA_BLANK_N, VGA_CLK, VGA_HS, VGA_SYNC_N, VGA_VS,
18                FPGA_I2C_SCLK, FPGA_I2C_SDAT, AUD_XCK, AUD_DACLCK, AUD_ADCLCK, AUD_BCLK,
19                AUD_ADCDAT, AUD_DACDAT);
20
21 // DE1_SoC hardware
22 output logic [6:0] HEX0, HEX1, HEX2, HEX3, HEX4, HEX5;
23 output logic [9:0] LEDR;
24 input logic [3:0] KEY;
25 input logic [9:0] SW;
26
27 // DE1_SoC drivers for VGA
28 input CLOCK_50, CLOCK2_50;
29 output [7:0] VGA_R;
30 output [7:0] VGA_G;
31 output [7:0] VGA_B;
32 output VGA_BLANK_N;
33 output VGA_CLK;
34 output VGA_HS;
35 output VGA_SYNC_N;
36 output VGA_VS;
37
38 // I2C Audio/Video config interface
39 output FPGA_I2C_SCLK;
40 inout FPGA_I2C_SDAT;
41 // Audio CODEC
42 output AUD_XCK;
43 input AUD_DACLCK, AUD_ADCLCK, AUD_BCLK;
44 input AUD_ADCDAT;
45 output AUD_DACDAT;
46
47 // Make system resettable with key0
48 logic reset;
49 assign reset = ~KEY[0];
50
51 // Instantiate vga driver module
52 logic [9:0] x;
53 logic [8:0] y;
54 logic [7:0] r, g, b;
55 video_driver #(C.WIDTH(640), .HEIGHT(480))
56 v1 (.CLOCK_50, .reset, .x, .y, .r, .g, .b,
57    .VGA_R, .VGA_G, .VGA_B, .VGA_BLANK_N,
58    .VGA_CLK, .VGA_HS, .VGA_SYNC_N, .VGA_VS);
59
60 // Logic units to drive audio modules
61 logic read_ready, write_ready, read, write;
62 logic signed [23:0] readdata_left, readdata_right;
63 logic signed [23:0] writedata_left, writedata_right;
64 logic signed [23:0] noisy_left, noisy_right;
65
66 // Outputs the input audio
67 assign writedata_left = readdata_left;
68 assign writedata_right = readdata_right;
69 // Only read or write when both are possible
70 assign read = read_ready & write_ready;
71 assign write = read_ready & write_ready;
72
73 // Instantiate audio modules
74 clock_generator my_clock_gen(CLOCK2_50, 1'b0, AUD_XCK);
75 audio_and_video_config cfg(CLOCK_50, 1'b0, FPGA_I2C_SDAT, FPGA_I2C_SCLK);
76 audio_codec codec(CLOCK_50, 1'b0, read, write, writedata_left, writedata_right,
77    AUD_ADCDAT, AUD_BCLK, AUD_ADCLCK, AUD_DACLCK, read_ready, write_ready,
78    readdata_left, readdata_right, AUD_DACDAT);
79
80 // Instantiate audio segment averaging to be shifted into bar modules
81 logic [23:0] amps [0:19];
82 audio_averaging_shift #(3) aas (.clk(CLOCK_50), .rst(reset), .amps, .rL(readdata_left), .rR(readdata_right));
83
84 // Create 20 different bars to visually represent audio
85 logic [7:0] r1, g1, b1;
86 bar_drawer bar_1 (.clk(CLOCK_50), .rst(reset), .x, .y, .amp(amps[0]), .rOut(r1), .gOut(g1), .bOut(b1));
87
88 logic [7:0] r2, g2, b2;
89 bar_drawer bar_2 (.clk(CLOCK_50), .rst(reset), .x, .y, .amp(amps[1]), .rOut(r2), .gOut(g2), .bOut(b2));
90
```



```

90
91 logic [7:0] r3, g3, b3;
92 bar_drawer bar_3 (.clk(CLOCK_50), .rst(reset), .x, .y, .amp(amps[2]), .rOut(r3), .gOut(g3), .bOut(b3));
93
94 logic [7:0] r4, g4, b4;
95 bar_drawer bar_4 (.clk(CLOCK_50), .rst(reset), .x, .y, .amp(amps[3]), .rOut(r4), .gOut(g4), .bOut(b4));
96
97 logic [7:0] r5, g5, b5;
98 bar_drawer bar_5 (.clk(CLOCK_50), .rst(reset), .x, .y, .amp(amps[4]), .rOut(r5), .gOut(g5), .bOut(b5));
99
100 logic [7:0] r6, g6, b6;
101 bar_drawer bar_6 (.clk(CLOCK_50), .rst(reset), .x, .y, .amp(amps[5]), .rOut(r6), .gOut(g6), .bOut(b6));
102
103 logic [7:0] r7, g7, b7;
104 bar_drawer bar_7 (.clk(CLOCK_50), .rst(reset), .x, .y, .amp(amps[6]), .rOut(r7), .gOut(g7), .bOut(b7));
105
106 logic [7:0] r8, g8, b8;
107 bar_drawer bar_8 (.clk(CLOCK_50), .rst(reset), .x, .y, .amp(amps[7]), .rOut(r8), .gOut(g8), .bOut(b8));
108
109 logic [7:0] r9, g9, b9;
110 bar_drawer bar_9 (.clk(CLOCK_50), .rst(reset), .x, .y, .amp(amps[8]), .rOut(r9), .gOut(g9), .bOut(b9));
111
112 logic [7:0] r10, g10, b10;
113 bar_drawer bar_10 (.clk(CLOCK_50), .rst(reset), .x, .y, .amp(amps[9]), .rOut(r10), .gOut(g10), .bOut(b10));
114
115 logic [7:0] r11, g11, b11;
116 bar_drawer bar_11 (.clk(CLOCK_50), .rst(reset), .x, .y, .amp(amps[10]), .rOut(r11), .gOut(g11), .bOut(b11));
117
118 logic [7:0] r12, g12, b12;
119 bar_drawer bar_12 (.clk(CLOCK_50), .rst(reset), .x, .y, .amp(amps[11]), .rOut(r12), .gOut(g12), .bOut(b12));
120
121 logic [7:0] r13, g13, b13;
122 bar_drawer bar_13 (.clk(CLOCK_50), .rst(reset), .x, .y, .amp(amps[12]), .rOut(r13), .gOut(g13), .bOut(b13));
123
124 logic [7:0] r14, g14, b14;
125 bar_drawer bar_14 (.clk(CLOCK_50), .rst(reset), .x, .y, .amp(amps[13]), .rOut(r14), .gOut(g14), .bOut(b14));
126
127 logic [7:0] r15, g15, b15;
128 bar_drawer bar_15 (.clk(CLOCK_50), .rst(reset), .x, .y, .amp(amps[14]), .rOut(r15), .gOut(g15), .bOut(b15));
129
130 logic [7:0] r16, g16, b16;
131 bar_drawer bar_16 (.clk(CLOCK_50), .rst(reset), .x, .y, .amp(amps[15]), .rOut(r16), .gOut(g16), .bOut(b16));
132
133 logic [7:0] r17, g17, b17;
134 bar_drawer bar_17 (.clk(CLOCK_50), .rst(reset), .x, .y, .amp(amps[16]), .rOut(r17), .gOut(g17), .bOut(b17));
135
136 logic [7:0] r18, g18, b18;
137 bar_drawer bar_18 (.clk(CLOCK_50), .rst(reset), .x, .y, .amp(amps[17]), .rOut(r18), .gOut(g18), .bOut(b18));
138
139 logic [7:0] r19, g19, b19;
140 bar_drawer bar_19 (.clk(CLOCK_50), .rst(reset), .x, .y, .amp(amps[18]), .rOut(r19), .gOut(g19), .bOut(b19));
141
142 logic [7:0] r20, g20, b20;
143 bar_drawer bar_20 (.clk(CLOCK_50), .rst(reset), .x, .y, .amp(amps[19]), .rOut(r20), .gOut(g20), .bOut(b20));
144
145 // Draw to the VGA
146 always_ff @(posedge CLOCK_50) begin
147     if (x > 0 && x < 31) begin
148         r <= r1;
149         g <= g1;
150         b <= b1;
151     end else if (x > 32 && x < 63) begin
152         r <= r2;
153         g <= g2;
154         b <= b2;
155     end else if (x > 64 && x < 95) begin
156         r <= r3;
157         g <= g3;
158         b <= b3;
159     end else if (x > 96 && x < 127) begin
160         r <= r4;
161         g <= g4;
162         b <= b4;
163     end else if (x > 128 && x < 159) begin
164         r <= r5;
165         g <= g5;
166         b <= b5;
167     end else if (x > 160 && x < 191) begin
168         r <= r6;
169         g <= g6;
170         b <= b6;
171     end else if (x > 192 && x < 223) begin
172         r <= r7;
173         g <= g7;
174         b <= b7;
175     end else if (x > 224 && x < 255) begin
176         r <= r8;
177         g <= g8;
178         b <= b8;
179     end else if (x > 256 && x < 287) begin

```

```

180         r <= r9;
181         g <= g9;
182         b <= b9;
183     end else if (x > 288 && x < 319) begin
184         r <= r10;
185         g <= g10;
186         b <= b10;
187     end else if (x > 320 && x < 351) begin
188         r <= r11;
189         g <= g11;
190         b <= b11;
191     end else if (x > 352 && x < 383) begin
192         r <= r12;
193         g <= g12;
194         b <= b12;
195     end else if (x > 384 && x < 415) begin
196         r <= r13;
197         g <= g13;
198         b <= b13;
199     end else if (x > 416 && x < 447) begin
200         r <= r14;
201         g <= g14;
202         b <= b14;
203     end else if (x > 448 && x < 479) begin
204         r <= r15;
205         g <= g15;
206         b <= b15;
207     end else if (x > 480 && x < 511) begin
208         r <= r16;
209         g <= g16;
210         b <= b16;
211     end else if (x > 512 && x < 543) begin
212         r <= r17;
213         g <= g17;
214         b <= b17;
215     end else if (x > 544 && x < 575) begin
216         r <= r18;
217         g <= g18;
218         b <= b18;
219     end else if (x > 576 && x < 607) begin
220         r <= r19;
221         g <= g19;
222         b <= b19;
223     end else if (x > 608 && x < 639) begin
224         r <= r20;

```

```

225         g <= g20;
226         b <= b20;
227     end else begin
228         r <= SW[7:0];
229         g <= '0;
230         b <= '0;
231     end
232 end
233
234
235 // Turn off hex displays
236 assign HEX0 = '1;
237 assign HEX1 = '1;
238 assign HEX2 = '1;
239 assign HEX3 = '1;
240 assign HEX4 = '1;
241 assign HEX5 = '1;
242
243 endmodule
244

```

1.B - height_picker.sv

```
1 // Hunter North and Peter Zhong
2 // 05/26/2021
3 // EE 371
4 // Lab 6
5 //
6 // Module that will output the correct height based off an audio segment
7 // Parameters Used:
8 //   amp      - Amplitude of sound to be visually represented by bar
9 //   height   - Decided height of bar
10 module height_picker(amp, height);
11
12     input logic [23:0] amp;          // Dimension might need to be adjusted
13
14     output logic [8:0] height;
15
16     // Scale amp by 480
17     integer scaled_amp;
18     assign scaled_amp = amp * 23'h0111E0;
19
20     // Divide amp down by max of 24 bit number
21     logic [23:0] shrunk_amp;
22     assign shrunk_amp = scaled_amp / 24'hffffff;
23
24     // Assign final height
25     assign height = 480 - shrunk_amp;
26
27 endmodule
28
29 // Module to test the height_picker module
30 module height_picker_testbench();
31
32     logic [23:0] amp;          // Dimension might need to be adjusted
33     logic [8:0] height;
34
35     height_picker dut (.*);
36
37     initial begin
38         amp <= 24'hbf155c; #10;
39         amp <= 24'he4835d; #10;
40         amp <= 24'h009ed0; #10;
41     end
42 endmodule
```

1.C - color_picker.sv

```
1 // Hunter North and Peter Zhong
2 // 05/26/2021
3 // EE 371
4 // Lab 6
5 //
6 // Module that will output the correct color based off of audio segment
7 // Parameters Used:
8 //   amp      - Amplitude of sound to be visually represented by bar
9 //   rOut     - Amount of red coloring in output color
10 //   gOut     - Amount of green coloring in output color
11 //   bOut     - Amount of blue coloring in output color
12
13 module color_picker(amp, rOut, gOut, bOut);
14     input logic [23:0] amp;          // Dimension might need to be adjusted
15
16     output logic [7:0] rOut, gOut, bOut;
17
18     assign rOut = amp[23:16];
19     assign bOut = amp[15:8];
20     assign gOut = amp[7:0];
21
22 endmodule
23
24 // Module to test the color_picker module
25 module color_picker_testbench();
26
27     logic [23:0] amp;          // Dimension might need to be adjusted
28     logic [7:0] rOut, gOut, bOut;
29
30     color_picker dut (.*);
31
32     initial begin
33         amp <= 24'hfff010; #10;
34         amp <= 24'h0ff111; #10;
35         amp <= 24'h00f0d4; #10;
36     end
37 endmodule
```

1.D - bar_drawer.sv

```
1 // Hunter North and Peter Zhong
2 // 05/26/2021
3 // EE 371
4 // Lab 6
5 //
6 // Module that will draw a bar on the screen based on an audio segment
7 // Parameters Used:
8 //   clk      - Clock to coordinate timing in module
9 //   rst      - Signal to reset bar to all black
10 //   x        - X component of location that is being drawn to
11 //   y        - Y component of location that is being drawn to
12 //   amp      - Amplitude of sound to be visually represented by bar
13 //   rOut     - Red coloring in bar
14 //   gOut     - Green coloring in bar
15 //   bOut     - Blue coloring in bar
16 module bar_drawer (clk, rst, x, y, amp, rOut, gOut, bOut);
17
18     input logic      clk;
19     input logic      rst;
20     input logic [9:0] x;
21     input logic [8:0] y;
22     input logic [23:0] amp;          // Dimension might need to be adjusted
23
24     output logic [7:0] rOut, gOut, bOut;
25
26     /***Determine Height of Bar***/
27     logic [8:0] height;
28     height_picker hp (.x);
29
30
31     /***Determine Color of Bar***/
32     logic [7:0] rBar, gBar, bBar;
33     color_picker cp (.amp, .rOut(rBar), .gOut(gBar), .bOut(bBar));
34
35     /***Draw to Board ***/
36     always_ff @(posedge clk) begin
37         // Black when resetting
38         if (rst) begin
39             rOut <= '0;
40             gOut <= '0;
41             bOut <= '0;
42             // Black if outside the determined bar height
43         end else if (y < height) begin
44             rOut <= '0;
45             gOut <= '0;
46             bOut <= '0;
47             // Draw bar calculated colors if inside bar height
48         end else if (y >= height) begin
49             rOut <= rBar;
50             gOut <= gBar;
51             bOut <= bBar;
52         end
53     end
54 endmodule
```

```

55
56 // Module to test the bar_drawer module
57 module bar_drawer_testbench ();
58
59 // Inputs to drive dut
60 logic      clk;
61 logic      rst;
62 logic [9:0] x;
63 logic [8:0] y;
64 logic [23:0] amp;      // Dimension might need to be adjusted
65
66 // Outputs for dut
67 logic [7:0] rOut, gOut, bOut;
68
69 // Simulated clock for testing
70 parameter clock_period = 100;
71 initial begin
72     clk <= 0;
73     forever #(clock_period / 2) clk <= ~clk;
74 end
75
76 // Instantiate module for testing
77 bar_drawer dut (.*);
78
79 // Test dut
80 initial begin
81     // Set defaults
82     rst <= 0;  x <= 0;  y <= 0;  amp <= 0;      @(posedge clk);
83
84     // Reset system
85     rst <= 1;                                     repeat(1)@(posedge clk);
86
87     // Undo reset
88     rst <= 0;                                     repeat(1)@(posedge clk);
89
90     // Test large (250) amp
91     // inside bar...
92     y <= 400;  amp <= 8000000;                    repeat(2)@(posedge clk);
93     // Outside bar...
94     y <= 100;                                     repeat(2)@(posedge clk);
95
96     $stop;
97 end
98 endmodule

```

1.E - audio_averaging_shift.sv

```
1 // Hunter North and Peter Zhong
2 // 05/26/2021
3 // EE 371
4 // Lab 6
5
6 // Module that will calculate the average value over a set of audio samples. This module
7 // will store 20 difference averages in a shift register that will continually shift right
8 // in order to make room for the newest average.
9 // Parameters required:
10 // UPDATE_FREQ - The rate at which we are shifting in the newest average value
11 // clk - Signal to coordinate timing in module
12 // rst - Signal to reset the module
13 // rL - The right amplitude from audio file
14 // rR - The left amplitude from audio file
15 // amps - A 20 unit structure which stores the previous 20 amplitudes
16
17 module audio_averaging_shift #(parameter UPDATE_FREQ = 5) (clk, rst, amps, rL, rR);
18
19     input logic clk, rst;
20     input logic [23:0] rL, rR;
21     output logic [23:0] amps [0:19];
22
23     // control logic for updating average value and shifting registers
24     integer count;
25     logic update_avg, shift_enable;
26
27     always_ff @(posedge clk) begin
28         if (rst) begin
29             count <= 1;
30             update_avg <= 0;
31             shift_enable <= 0;
32         end
33         // update avg one cycle before shifting registers
34         else if (count + 1 == 50000000 / UPDATE_FREQ) begin
35             count <= count + 1;
36             update_avg <= 1;
37             shift_enable <= 0;
38         end
39         else if (count == 50000000 / UPDATE_FREQ) begin
40             count <= 1;
41             update_avg <= 0;
42             shift_enable <= 1;
43         end
44         else begin
45             count <= count + 1;
46             shift_enable <= 0;
47             update_avg <= 0;
48         end
49     end
50 end
```

```

50
51
52 // audio averaging, update average
53 logic [23:0] curr_avg, avg;
54 integer samples; // number of samples to average for every update operation
55 // assign samples = 48000 / UPDATE_FREQ; // 48k samples per second
56 // for testbench
57 assign samples = 5000000 / UPDATE_FREQ;
58
59 always_ff @(posedge clk) begin
60     if (rst) begin
61         curr_avg <= 0;
62         avg <= 0;
63     end
64     else if (update_avg) begin
65         avg <= curr_avg;
66         curr_avg <= (rL / samples) + (rR / samples);
67     end
68     else
69         curr_avg <= curr_avg + (rL / samples) + (rR / samples);
70 end
71
72
73
74 // shift registers w/ count, update frequency 0.2s
75 always_ff @(posedge clk) begin
76     if (rst) begin
77         amps <= '{default: '0};
78     end
79     else if (shift_enable) begin
80         amps[19] <= amps[18];
81         amps[18] <= amps[17];
82         amps[17] <= amps[16];
83         amps[16] <= amps[15];
84         amps[15] <= amps[14];
85         amps[14] <= amps[13];
86         amps[13] <= amps[12];
87         amps[12] <= amps[11];
88         amps[11] <= amps[10];
89         amps[10] <= amps[9];
90         amps[9] <= amps[8];
91         amps[8] <= amps[7];
92         amps[7] <= amps[6];
93         amps[6] <= amps[5];
94         amps[5] <= amps[4];
95         amps[4] <= amps[3];
96         amps[3] <= amps[2];
97         amps[2] <= amps[1];
98         amps[1] <= amps[0];
99         amps[0] <= avg;
100     end
101 end
102
103 endmodule

```



```

106 // Module to test the audio_averaging_shift module
107 module audio_averaging_shift_testbench();
108     logic clk, rst;
109     logic [23:0] rL, rR;
110     logic [23:0] amps [0:19];
111
112     // shifting once every 2 cycles
113     audio_averaging_shift #(1000000) dut(.);
114
115     // Setting up a simulated clock.
116     parameter CLOCK_PERIOD = 100;
117     initial begin
118         clk <= 0;
119         forever #(CLOCK_PERIOD/2) clk <= ~clk; // Forever toggle the clock
120     end
121
122     initial begin
123         rst <= 1; rL <= 0; rR <= 0; repeat(5) @(posedge clk);
124         rst <= 0; rL <= 50; rR <= 50; @(posedge clk);
125         rL <= 100; rR <= 100; @(posedge clk);
126         rL <= 150; rR <= 150; @(posedge clk);
127         rL <= 200; rR <= 200; @(posedge clk);
128         rL <= 250; rR <= 250; @(posedge clk);
129         rL <= 300; rR <= 300; @(posedge clk);
130
131         rL <= 50; rR <= 50; @(posedge clk);
132         rL <= 100; rR <= 100; @(posedge clk);
133         rL <= 150; rR <= 150; @(posedge clk);
134         rL <= 200; rR <= 200; @(posedge clk);
135         rL <= 250; rR <= 250; @(posedge clk);
136         rL <= 300; rR <= 300; @(posedge clk);
137
138         rL <= 50; rR <= 50; @(posedge clk);
139         rL <= 100; rR <= 100; @(posedge clk);
140         rL <= 150; rR <= 150; @(posedge clk);
141         rL <= 200; rR <= 200; @(posedge clk);
142         rL <= 250; rR <= 250; @(posedge clk);
143         rL <= 300; rR <= 300; @(posedge clk);
144
145         rL <= 50; rR <= 50; @(posedge clk);
146         rL <= 100; rR <= 100; @(posedge clk);
147         rL <= 150; rR <= 150; @(posedge clk);
148         rL <= 200; rR <= 200; @(posedge clk);
149         rL <= 250; rR <= 250; @(posedge clk);
150         rL <= 300; rR <= 300; @(posedge clk);
151
152         rL <= 50; rR <= 50; @(posedge clk);
153         rL <= 100; rR <= 100; @(posedge clk);
154         rL <= 150; rR <= 150; @(posedge clk);
155         rL <= 200; rR <= 200; @(posedge clk);
156         rL <= 250; rR <= 250; @(posedge clk);
157         rL <= 300; rR <= 300; @(posedge clk);
158
159         rL <= 50; rR <= 50; @(posedge clk);
160         rL <= 100; rR <= 100; @(posedge clk);
161         rL <= 150; rR <= 150; @(posedge clk);
162         rL <= 200; rR <= 200; @(posedge clk);
163         rL <= 250; rR <= 250; @(posedge clk);
164         rL <= 300; rR <= 300; @(posedge clk);
165     end
166     $stop;
167 endmodule

```